



**Tshwane University
of Technology**

We empower people

**Tshwane University of Technology
2024 SEMESTER 2 TEST 1**

SUBJECT: ELECTRONICS II

SUBJECT CODE: EL2F06D/EL2116D

PAPER NO.: PAPER 1

PAPER DESCRIPTION: CLOSED BOOK

DURATION: 2 HOUR

SPECIAL REQUIREMENTS:	(✓)
None	
Non-programmable pocket calculators	
Scientific calculators	✓
Drawing instruments	
Other	

INSTRUCTIONS TO CANDIDATES:

Answer all questions. All calculations must be shown. Write answers in the spaces provided on the question paper. Use opposite pages for calculations. Do not do calculations inside blocks intended for answers. All answers must be given in correct units. All silicon junction voltages are 0,7 V in forward bias. Answers must be accurate to the first three significant figures.

NUMBER OF PAGES: 6 (Including this page)

ANNEXURES: NONE

QUALIFICATION(S):

N DIP: COMPUTER SYSTEMS ENG.

EXAMINER: MR TD MATSHIBA

MODERATOR: MR TC TSHIPOTA

TOTAL MARKS: 49

FULL MARKS: 45

Initials:	Surname: MEMO	Student No:
		0000000000

Q1

1) $Z_0 = ?$

$$V_{R_L} = V_{S1} \frac{R_L}{R_L + Z_0}$$
$$400\text{m} = 750\text{m} \frac{100}{100 + Z_0}$$

$$100 + Z_0 = \frac{750}{400} \cdot 100$$

$$Z_0 = 187,5 - 100$$
$$= 87,5 \Omega$$

2) $A_{V_{NL}} = \frac{V_o}{V_i} = \frac{750\text{m}}{50\text{m}}$

$$= 15$$

3) $A_{V_L} = \frac{V_o}{V_i} = \frac{400\text{m}}{50\text{m}}$

4) $V_{Z_i} = V_{S2} \frac{Z_i}{Z_i + R_s}$

$$750\text{m} = 75\text{m} \frac{Z_i}{Z_i + 1000}$$

$$Z_i + 1000 = \frac{75\text{m}}{50\text{m}} Z_i$$

$$1000 = 1,5 Z_i - Z_i$$

$$1000 = 0,5 Z_i$$

$$Z_i = 2000 \Omega$$

5) $A_I = \frac{V_o/R_L}{V_i/Z_i} = \frac{V_o Z_i}{V_i R_L}$

$$= 8 \frac{2000}{100}$$

$$= 160$$

6) $I = \frac{V_{R_L}}{R_L} = \frac{400\text{m}}{100}$


$$= 4\text{mA}$$

7) $\text{dB} = 20 \log A_{V_L}$

$$= 20 \log 8$$
$$= 18,06 \text{ dB}$$

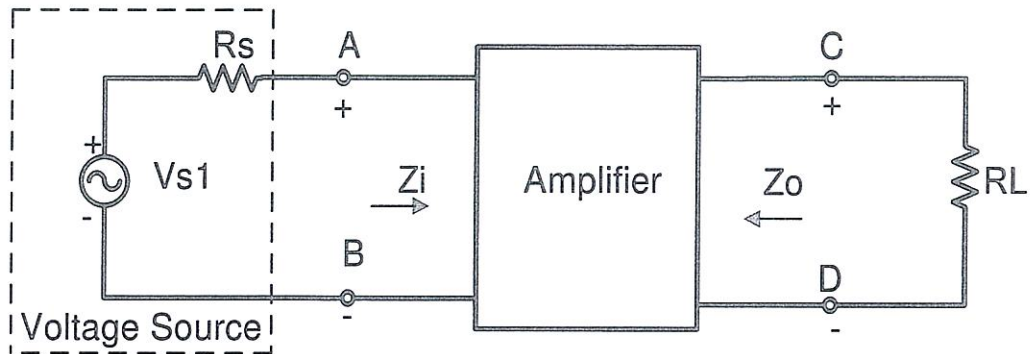QUESTION 1 [7]

In the circuit below, the voltage between A and B is 50mV RMS and that between C and D is 400mV RMS. If the load R_L is disconnected and there is an open circuit between C and D, the voltage between C and D rises to 750mV RMS. R_L is 100Ω and R_s is $1k\Omega$.



Determine the following:

The value of Z_o :	87,5 Ω .
The Voltage Gain of Amplifier 1 with R_L disconnected (open circuit between C and D):	15 15
The Voltage Gain of Amplifier 1 with R_L connected (as it is shown in the circuit diagram):	8
The value of Z_i , if the voltage rises to 75mV RMS between A and B if Amplifier 1 is disconnected from A and B :	2000 Ω .
The Current Gain of Amplifier 1 with R_L connected (as it is shown in the circuit diagram)	160
The RMS current value flowing at point C with the load resistor R_L connected, as it is shown in the circuit diagram:	4 mA
The voltage gain of Amplifier 1 in decibel with the load R_L connected (as it is shown in the circuit diagram), given $\text{dB} = 20 \log V_{out} / V_{in}$	18,06 dB.

Q2

$$\begin{aligned} 1) V_{s1_{RMS}} &= \frac{V_{Peak}}{\sqrt{2}} \\ &= \frac{15m}{\sqrt{2}} \\ &= 10,61mV \end{aligned}$$

$$\begin{aligned} 2) F &= \frac{1}{T} \\ &= \frac{1}{200\mu s} \\ &= 5000Hz \\ &= 5kHz. \end{aligned}$$

$$\begin{aligned} 3) V_{R1} &= V_{s1} \frac{R_1}{R_1 + R_5} \\ 10m &= 15m \frac{R_1}{R_1 + 100} \end{aligned}$$

$$R_1 + 100 = \frac{15m}{10m} R_1$$

$$\therefore R_1 = 200\Omega.$$

$$\begin{aligned} 4) I_{Peak} &= \frac{V_{R1}}{R_1} \\ &= \frac{10m}{200} \\ &= 50\mu A \end{aligned}$$

$$\begin{aligned} I_{RMS} &= \frac{I_{Peak}}{\sqrt{2}} = \frac{50\mu}{\sqrt{2}} \\ &= 35,36\mu A. \end{aligned}$$


$$\begin{aligned} 5) dB &= 20 \log \frac{V_o}{V_i} \\ &= 20 \log \frac{10m}{15m} \\ &= -3,52 dB. \end{aligned}$$

$$\begin{aligned} 6) V_{R1} &= V_{s1} \frac{R_1}{R_1 + R_5} \\ 1m &= 10,61m \frac{R_1}{R_1 + 100} \\ R_1 + 100 &= \frac{10,61m}{1m} R_1 \\ R_1 &= 10,41\Omega \end{aligned}$$

$$\begin{aligned} 7) I &= \frac{V_{s1}}{R_1 + R_5} \\ &= \frac{10,61m}{0 + 100} \\ &= 0,106mA \\ &= 106\mu A. \end{aligned}$$



$$\begin{aligned} 8) P &= VI \\ &= V_{s1} I_{s1} \\ &= 10,61m \times 106\mu \\ &= 1,125\mu W. \end{aligned}$$

QUESTION 2 [8]

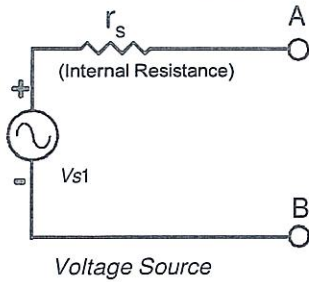


In the circuit on the left, the voltage between A and B is shown in the oscilloscope on the right. V_{s1} is a voltage source with internal resistance r_s .

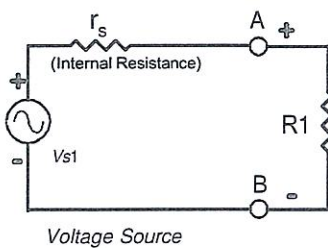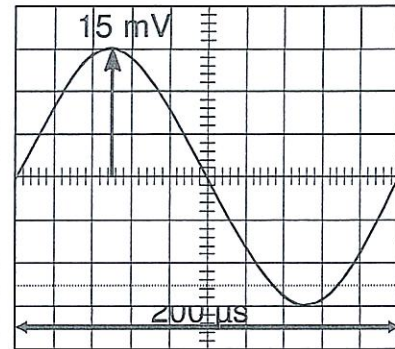When a resistor R_1 is connected to the circuit, as shown in the next circuit, the voltage between A and B changes to that shown in the next oscilloscope screen:



r_s is 100Ω

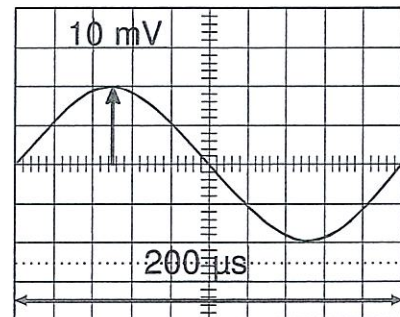

Determine the following for V_s and R_1 :

The RMS voltage value of the voltage source V_{s1} with no load resistor, assuming it is a pure sine wave:	10,61 mV
The frequency of the voltage source V_{s1} with no load resistor:	5 KHz
The value of the load resistor R_1 , using the difference between the two oscilloscope traces:	200 Ω
The RMS current value flowing at point A with the load resistor R_1 connected, assuming it is a pure sine wave:	35,36 μA
The voltage ratio in decibel between points A and B with no load connected versus that with the load R_1 connected,	- 3,52 dB
The value of the load resistor R_1 , if the voltage between A and B would be 1 millivolt RMS	10,41 Ω
The RMS current value flowing at point A with the load resistor R_1 replaced by a short circuit, assuming it is a pure sine wave:	106 μA
The RMS power wasted in the voltage source with the load resistor R_1 replaced by a short circuit, assuming it is a pure sine wave:	1,125 μW

53

$$1) \quad V_{R2} = 15 \frac{6,8K}{6,8K + 33K} = 2,563V$$

$$ii) \quad V_E = V_{R2} - V_{BE} = 2,563 - 0,7 = 1,863V$$

$$iii) \quad I_E = \frac{V_E}{R_{E1} + R_{E2}} = \frac{1,863}{270 + 390} = 2,82mA$$

$$2) \quad h_{ib} = \frac{25m}{2,82m} = 8,865\Omega$$

$$3) \quad h_{ie} = h_{fe} \cdot h_{ib} = 180 \times 8,865 = 1595,7$$

$$4) \quad Z_o = R_L = 1800\Omega = 1,8k$$

$$5) \quad i) \quad R_{BB} = R_1 // R_2 = 33K // 6,8K = 5638\Omega$$

$$ii) \quad Z_b = h_{ie} + (h_{fe} + 1)R_{E1} = 1595,7 + (180 + 1)270 = 50465,7\Omega$$

$$iii) \quad Z_i = R_{BB} // Z_b = 5638 // 50465,7 = 5071\Omega = 5,071K\Omega$$

$$6) \quad A_{V_{NL}} = - \frac{h_{fe} R_c}{h_{ie} + (h_{fe} + 1)R_{E1}} = - \frac{180 \times 1800}{50465,7} = -6,42$$

$$7) \quad A_{V_L} = A_{V_{NL}} \frac{R_L}{R_L + R_c} = -6,42 \frac{12K}{12K + 1,8K} = -5,58$$


$$8) \quad dB = 20 \log A_{V_L} = 20 \log 5,58 = 14,93dB$$

$$9) \quad A_{V_s} = A_{V_L} \frac{Z_i}{Z_i + R_s} = -5,58 \frac{5071}{5071 + 200} = -5,35$$

$$10) \quad A_{V_s} dB = 20 \log A_{V_s} = 20 \log 5,35 = 14,57$$

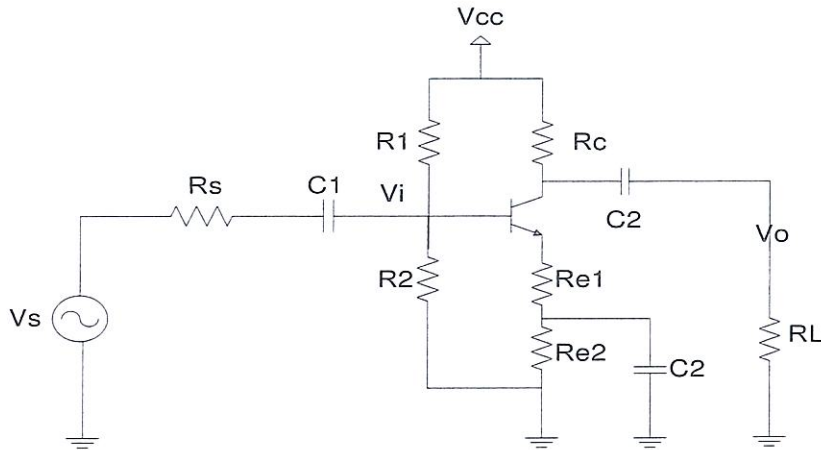
QUESTION 3 [14]

For the circuit below, $V_{cc} = 15V$, $R_1 = 33\text{ k}\Omega$, $R_2 = 6.8\text{ k}\Omega$, $R_c = 1.8\text{ k}\Omega$, $1/h_{oe} = \text{very large}$, $R_s = 220\text{ }\Omega$, $R_{e1} = 270\text{ }\Omega$, $R_{e2} = 390\text{ }\Omega$, $R_L = 12\text{ k}\Omega$ and $h_{fe} = 180$
 $h_{ib} = 25\text{ mV} \div I_E$; $h_{ie} = h_{fe} \times h_{ib}$



3.1 Sketch the small-signal equivalent model for the circuit in above.

(4)

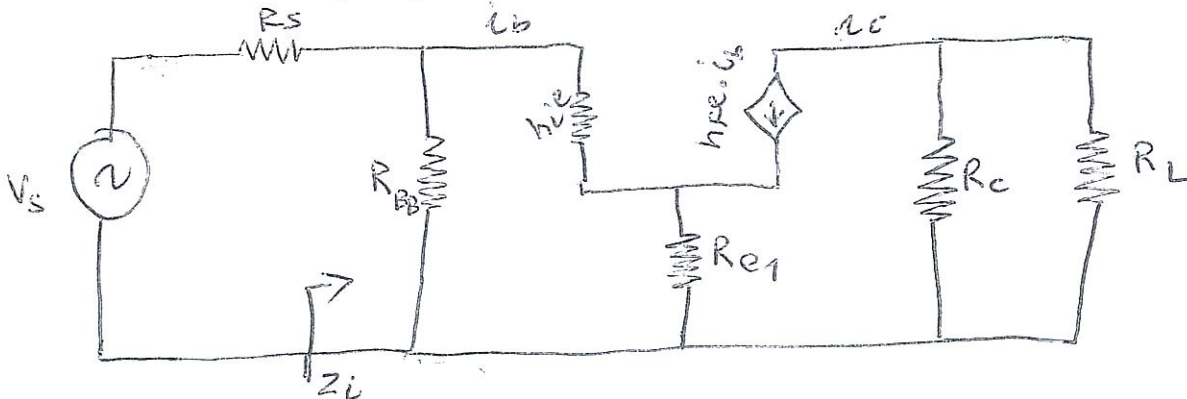

3.2 Complete the following table:

I_E	2,82 mA	(1)	h_{ib}	8,865 Ω	(1)
h_{ie}	1595,6 Ω	(1)	Z_o	1,8 k	(1)
Z_{in}	5071 Ω	(1)	$A_{v\text{-unloaded}}$	-6,42	(1)
$A_{v\text{-loaded}}$	-5,58	(1)	$A_{v\text{-loaded}}(\text{dB})$	14,93 dB	(1)
A_{vs}	-5,35	(1)	$A_{vs}(\text{dB})$	14,57 dB	(1)

Q.4

$$1) i) V_{R2} = 10 \frac{18K}{18K + 22K}$$

$$= 4,5V$$

$$ii) V_E = 4,5 - 0,7$$

$$= 3,8V$$

$$iii) I_E = \frac{V_E}{R_E} = \frac{3,8}{1,5K}$$

$$= 2,53mA$$

$$2) h_{ib} = \frac{25m}{I_E} = \frac{25m}{2,53m}$$

$$= 9,88\Omega$$

$$3) h_{ie} = h_{fe} \cdot h_{ib}$$

$$= 200 \times 9,88$$

$$= 1976\Omega$$

$$4) i) Z_o = R_E // \frac{h_{ie} + R_{BB}}{h_{fe} + 1}$$

$$ii) R_{BB} = R_1 // R_2 = 22K // 18K$$

$$= 9,9K$$

$$= 9900\Omega$$

$$iii) \frac{h_{ie} + R_{BB}}{h_{fe} + 1} = \frac{1976 + 9900}{200 + 1}$$

$$= 59,08$$

$$\therefore iv) Z_o = 1500 // 59,08$$

$$= 56,84\Omega$$

$$5) i) Z_{iNL} = R_{BB} // Z_{bNL}$$

$$Z_{bNL} = h_{ie} + (h_{fe} + 1)R_E$$

$$= 1976 + (200 + 1)1500$$

$$= 303476\Omega$$

$$\therefore ii) Z_{iNL} = 9900 // 303476$$

$$= 9587\Omega$$

$$6) i) Z_{iL} = R_{BB} // Z_{bL}$$

$$ii) Z_{bL} = h_{ie} + (h_{fe} + 1)(R_E // R_L)$$

$$iii) R_E // R_L = 1500 // 1000$$

$$= 600\Omega$$

$$iv) Z_{bL} = 1976 + (200 + 1)600$$

$$= 122576\Omega$$

$$v) Z_{iL} = 9900 // 122576$$

$$= 9160\Omega$$

$$7) A_{VNL} = \frac{(h_{fe} + 1)R_E}{h_{ie} + (h_{fe} + 1)R_E}$$

$$= \frac{(200 + 1)1500}{303476}$$

$$= 0,993$$

$$8) A_{VL} = \frac{(h_{fe} + 1)(R_E // R_L)}{h_{ie} + (h_{fe} + 1)(R_E // R_L)}$$

$$= \frac{(200 + 1)600}{122576}$$

$$= 0,984$$

$$9) A_{VS} = A_{VL} \frac{Z_i}{Z_i + R_s}$$

$$= 0,984 \frac{9160}{9160 + 600}$$

$$= 0,923$$

$$(10) 2\pi F = 12,566 \times 10^3$$

$$F = 1999,9Hz$$

$$= 2KHz$$

$$11) V_{Speak} = 10 \times 10^{-3}$$

$$= 10mV$$

QUESTION 4 [14]

Fill in the answers into the blocks provided. Do not do calculations inside blocks intended for answers. You may be penalised for untidy work. Answers will not be marked **unless correct units are given**. All silicon junction voltages are 0,7 V in forward bias. Answers must be accurate to the first three significant figures.

$$h_{ib} = 25\text{mV} \div I_E; h_{ie} = h_{fe} \times h_{ib}$$


$$R_1 = 22\text{k}\Omega \quad R_2 = 18\text{k}\Omega$$

$$R_3 = 1,5\text{k}\Omega \quad R_L = 1\text{k}\Omega$$

$$V_s = 10 \times 10^{-3} \sin(12.566 \times 10^3 t)$$


$$R_s = 600\Omega \quad h_{fe} = 200$$
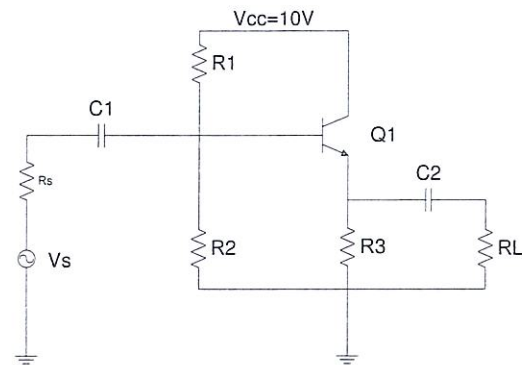
$$\text{Note } V_s = V_{\text{peak}} \sin 2\pi f t$$



4.1 Sketch the small-signal equivalent model for the circuit in above.

(4)

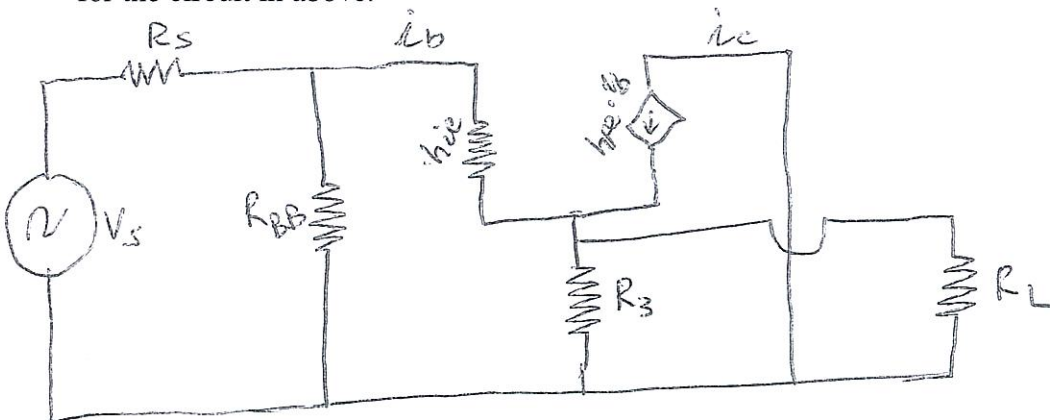

4.2 Complete the following table:

I_E	2,53 mA	(1)	h_{ie}	1976 Ω	(1)
$Z_{o-(\text{unloaded})}$	56,84 Ω	(1)	$Z_{i-(\text{unloaded})}$	9587 Ω	(1)
$Z_{i-(\text{loaded})}$	9160 Ω	(1)	$A_{v-\text{unloaded}}$	0,993	(1)
$A_{v-\text{loaded}}$	0,984	(1)	A_{vs}	0,923	(1)
Input frequency	2 KHz	(1)	$V_s (\text{peak})$	10 mV	(1)

Q5

$$\begin{aligned} 1) I_B &= \frac{V_{CC} - V_{BE}}{R_B} \\ &= \frac{60 - 0,7}{3,3 \times 10^6} \\ &= 17,97 \mu A. \end{aligned}$$

$$\begin{aligned} 2) V_B &= V_{BE} \\ &= 0,7 V. \end{aligned}$$

$$\begin{aligned} 3) I_C &= \beta I_B \\ &= 150 \times 17,97 \mu A \\ &= 2,696 mA \end{aligned}$$


$$\begin{aligned} 4) V_{R_B} &= V_{CC} - V_{BE} \\ &= 60 - 0,7 \\ &= 59,3 V \end{aligned}$$

$$\begin{aligned} 5) I_E &= I_B + I_C \\ &= 17,97 \mu A + 2696 \mu A \\ &= 2,714 mA. \end{aligned}$$

$$\begin{aligned} 6) V_{R_C} &= I_C R_C \\ &= 2,696 mA \times 1,2 K \\ &= 3,235 V \end{aligned}$$

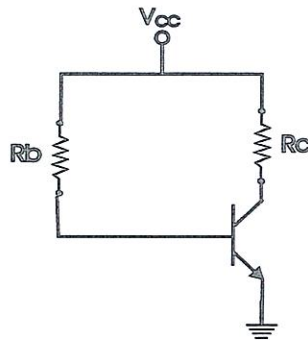QUESTION 5 [6]

Given: $V_{CC} = 60 \text{ V}$, $R_B = 3,3 \text{ M}\Omega$, $R_C = 1,2 \text{ k}\Omega$, $\beta_{dc} = 150$, $V_{BE} = 0,7 \text{ V}$



Fill in the table with respect to the above circuit.

I_B	$17,97 \mu A$	V_B	$0,7 \text{ V}$
I_C	$2,696 \text{ mA}$	V_{Rb}	$59,3 \text{ V}$
I_E	$2,714 \text{ mA}$	V_{RC}	$3,235 \text{ V}$