



**Tshwane University
of Technology**
We empower people

NAME

MEMO

STUDENT NUMBER

FORMATIVE ASSESSMENT 1 SEMESTER 2 2022

SUBJECT: ELECTRONICS II

SUBJECT CODE: ELC211B/EL2116D/EL2F06D

PAPER DESCRIPTION: CLOSED BOOK

DURATION: 2 HOURS

INSTRUCTIONS TO CANDIDATES:

Fill in the answers into the blocks provided. Do not do calculations inside blocks intended for answers. You may be penalized for untidy work. Answers will not be marked unless correct units are given. All silicon junction voltages are 0,7 V in forward bias. Answers must be accurate to the first three significant figures.

NUMBER OF PAGES: 5
NUMBER OF QUESTIONS: 4
APPENDICES: 0


EXAMINERS: MR T D MATSHIBA
MR I L MACHELE

MODERATOR: MRS Z MAHLOBOGWANE

TOTAL MARK: 47

FULL MARK 40

QUESTION 1 (10)

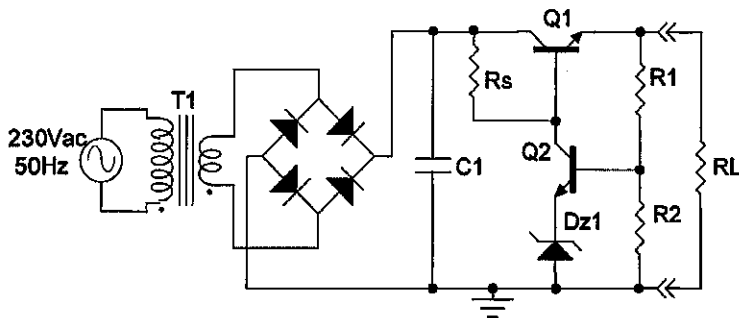

Load current through RL:
200mA
 V_{DC} (across C1) = 200 V
 $R_s = 3300 \Omega$
 $C1 = 470 \mu F$
 $R1 = 62 k\Omega$, $R2 = 2200 \Omega$
 $Dz1 = 5.1 V$
 $\beta(Q1) = 110$
 $\beta(Q2) = \text{LARGE}$ (Ignore $I_{B(Q2)}$)

**Answer the following
for the circuit given:**

(a) The purpose of the circuit is to provide a constant voltage across RL while the voltage across C1 may vary. Which component in the circuit is used as error amplifier to counteract changes in the output voltage?		Component label: Q ₂
(b) Explain the purpose of the following components: T1: ISOLATION STEP DOWN STEP UP		
C1: FILTER.		
(c) Calculate and fill in the following for the circuit given:		V(RL): 169,254V
I_{RS} : 9,105 mA	$I_{C(Q2)}$: 0,811 mA	$I_{C(Q1)}$: 200,81 mA
P(R1): 430,807 mW	P(R2): 15,289 mW	P(Q1): 6,174 W

QUESTION 1

$$\textcircled{1} V_{R_L} = V_{R_2} \frac{R_1 + R_2}{R_2}$$

$$\begin{aligned} \textcircled{2} V_{R_2} &= V_{BE_{Q_2}} + V_{Z1} \\ &= 0,7 + 5,1 \\ &= 5,8 \text{ V} \end{aligned}$$

$$\begin{aligned} \textcircled{3} V_{R_L} &= V_{R_2} \frac{R_1 + R_2}{R_2} \\ &= 5,8 \frac{62 \text{ K} + 2,2 \text{ K}}{2,2 \text{ K}} \\ &= 169,254 \text{ V} \end{aligned}$$

$$\begin{aligned} \textcircled{4} I_{R_1} &= I_{R_2} = \frac{V_{R_2}}{R_2} \\ &= \frac{5,8}{2,2} \\ &= 2,636 \text{ mA} \end{aligned}$$

$$\begin{aligned} \textcircled{5} V_{C1} &= V_{R_S} + V_{BE_{Q_1}} + V_{R_L} \\ 200 &= V_{R_S} + 0,7 + 169,254 \\ V_{R_S} &= 30,046 \text{ V} \end{aligned}$$

$$\begin{aligned} \textcircled{6} I_{R_S} &= \frac{V_{R_S}}{R_S} = \frac{30,046}{3300} \\ &= 9,105 \text{ mA} \end{aligned}$$

$$\begin{aligned} \textcircled{7} I_{E_{Q_1}} &= I_{R_1} + I_{R_L} \\ &= 2,636 \text{ mA} + 200 \text{ mA} \\ &= 202,636 \text{ mA} \end{aligned}$$

$$\begin{aligned} \textcircled{8} I_{B_{Q_1}} &= \frac{I_{E_{Q_1}}}{\beta_{Q_1} + 1} \\ &= \frac{202,636 \text{ mA}}{110 + 1} \\ &= 1,825 \text{ mA} \end{aligned}$$

$$\begin{aligned} \textcircled{9} I_{C_{Q_1}} &= \frac{\beta_{Q_1} I_{E_{Q_1}}}{\beta_{Q_1} + 1} \\ &= \frac{110 \times 202,636 \text{ mA}}{110 + 1} \\ &= 200,81 \text{ mA} \end{aligned}$$

$$\begin{aligned} \textcircled{10} I_{R_S} &= I_{B_{Q_1}} + I_{C_{Q_2}} \\ 2,636 \text{ mA} &= 1,825 \text{ mA} + I_{C_{Q_2}} \\ I_{C_{Q_2}} &= 0,811 \text{ mA} \end{aligned}$$

$$\begin{aligned} \textcircled{11} I_{C_{Q_2}} &= I_{E_{Q_2}} = I_{Z1} \\ &= 0,811 \text{ mA} \end{aligned}$$

$$\begin{aligned} \textcircled{12} V_{R_1} &= I_{R_1} R_1 \\ &= 2,636 \text{ mA} \times 62 \text{ K} \\ &= 163,432 \text{ V} \end{aligned}$$

$$\begin{aligned} \textcircled{13} P_{R_1} &= V_{R_1} I_{R_1} \\ &= 163,432 \times 2,636 \text{ mA} \\ &= 430,807 \text{ mW} \end{aligned}$$


$$\begin{aligned} \textcircled{14} P_{R_2} &= V_{R_2} I_{R_2} \\ &= 5,8 \times 2,636 \text{ mA} \\ &= 15,289 \text{ mW} \end{aligned}$$

$$\begin{aligned} \textcircled{15} V_{C1} &= V_{CE_{Q_1}} + V_{R_L} \\ 200 &= V_{CE_{Q_1}} + 169,254 \\ V_{CE_{Q_1}} &= 30,746 \text{ V} \end{aligned}$$

$$\begin{aligned} \textcircled{16} P_{Q_1} &= V_{CE_{Q_1}} I_{C_{Q_1}} \\ &= 30,746 \times 200,81 \text{ mA} \\ &= 6,174 \text{ W} \end{aligned}$$

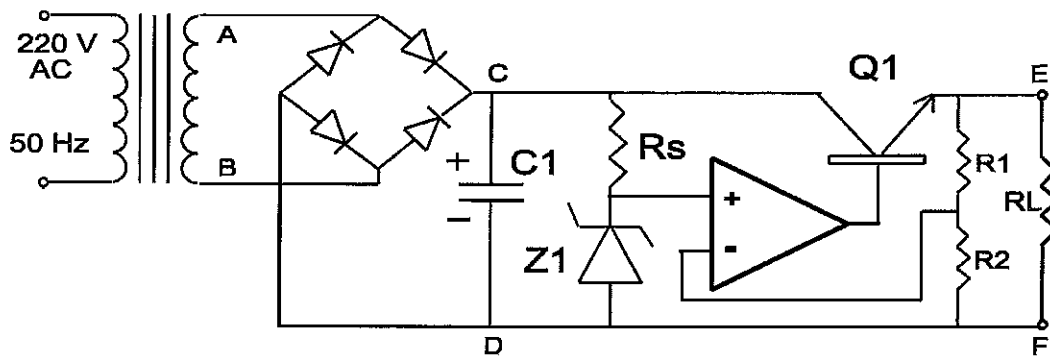QUESTION 2 (16)

Given: Load current through R_L : 600 mA The Op Amp is a TL071 (same pins as a 741)



The supply terminals (Pin 4 and 7) of the Op Amp is connected to D and C
Use $V_r(p-p) = I/CF$ when calculating ripple voltage

$$V_{C1} = 18 \text{ V}_{DC} \quad R_s = 2200\Omega$$

$$R_1 = 470\Omega$$

$$R_2 = 1000\Omega$$

$$C_1 = 2200\mu\text{F}$$

$$Z_1 = 5,6\text{V} / 1\text{W}$$

$$\beta_{Q1} = 90$$

$$Z_1 = 9\text{V} \text{ (1Watt Rated)}$$


Fill in:

The voltage across R_L : (2) 8,232 V	The voltage across R_1 : (2) 2,632 V
The emitter current ($I_{E(Q1)}$): (2) 605,6 mA	The current at the output of the Op Amp: (2) 6,655 mA
$V_{CE(Q1)}$: (2) 9,768 V	The peak-to-peak ripple voltage across C_1 : (2) 2,778 V (Include Zener and R_1 current)
By making R_1 adjustable, the output could be adjustable:	
What is the minimum output voltage if R_1 is an adjustable 470Ω ? (2) 5,6 V	What is the maximum output voltage if R_1 is an adjustable 470Ω ? (2) 8,232 V

QUESTION 2

- ① $V_{R_2} = V_{Z_1} = 5,6 \text{ V}$
- ② $I_{R_1} = I_{R_2} = \frac{V_{R_2}}{R_2} = \frac{5,6}{1000}$
 $= 5,6 \text{ mA}$
- ③ $V_{R_L} = V_{R_2} \frac{R_1 + R_2}{R_2}$
 $= 5,6 \frac{470 + 1000}{1000}$
 $= 8,232 \text{ V}$
- ④ $I_{E_{Q_1}} = I_{R_1} + I_{R_L}$
 $= 5,6 \text{ mA} + 600 \text{ mA}$
 $= 605,6 \text{ mA}$
- ⑤ $V_{R_1} = I_{R_1} R_1$
 $= 5,6 \text{ mA} \times 470$
 $= 2,632 \text{ V}$
- ⑥ $V_{C_1} = V_{CE_{Q_1}} + V_{R_L}$
 $18 = V_{CE_{Q_1}} + 8,232$
 $V_{CE_{Q_1}} = 9,768 \text{ V}$
- ⑦ $I_{B_{Q_1}} = \frac{I_{E_{Q_1}}}{\beta_{Q_1} + 1}$
 $= \frac{605,6 \text{ mA}}{90 + 1}$
 $= 6,655 \text{ mA}$

- ⑧ $I_{\text{out OpAmp}} = I_{B_{Q_1}}$
 $= 6,655 \text{ mA}$
- ⑨ $V_{R_5} = V_{C_1} - V_{Z_1}$
 $= 18 - 5,6$
 $= 12,4 \text{ V}$
- ⑩ $I_{R_5} = \frac{V_{R_5}}{R_5} = \frac{12,4}{2200}$
 $= 5,636 \text{ mA}$
- ⑪ $I_{R_5} = I_{Z_1}$
 $I_{Z_1} = 5,636 \text{ mA}$
- ⑫ $I_T = I_{Z_1} + I_{E_{Q_1}}$
 $= 5,636 \text{ mA} + 605,6 \text{ mA}$
 $= 611,236 \text{ mA}$
- ⑬ $V_{r(P-P)} = \frac{I}{C_F} = \frac{611,236 \times 10^{-3}}{2200 \times 10^{-6} \times 100}$
 $= 2,778 \text{ V}$
- ⑭ $V_{\text{out min}} = V_{R_2} \frac{R_{1 \text{ min}} + R_2}{R_2}$
 $= 5,6 \frac{0 + 1000}{1000}$
 $= 5,6 \text{ V}$
- ⑮ $V_{\text{out max}} = V_{R_2} \frac{R_{1 \text{ max}} + R_2}{R_2}$
 $= 5,6 \frac{470 + 1000}{1000}$
 $= 8,232 \text{ V}$

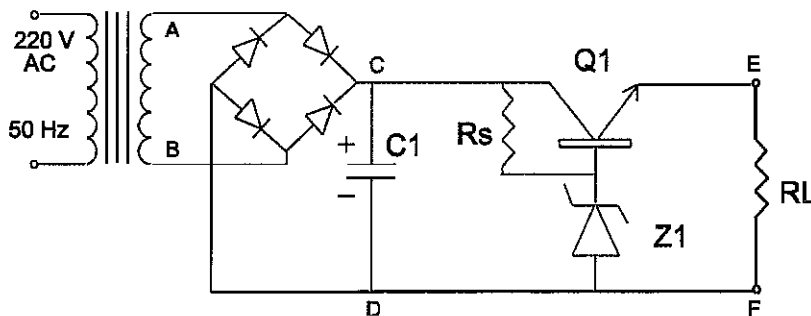QUESTION 3 (12)**Given:**

Load current
through R_L : 800
mA

Ripple voltage
across C_1 :
 $V_r(p-p) = I/CF$ or
 I/C
(Assume ripple is a
triangle wave)

$$V_{RMS}(AB) = 15V_{RMS}$$

$$R_s = 150$$

$$C_1 = 4700\mu F$$

The current through Z_1 is 40mA (with load current of 800mA)

$$Z_1 = 10V \text{ (1 Watt Rated)}$$

Fill in:

The average voltage across the load: 9,3V	The peak-to-peak ripple across C_1 : 1,787V (Include I_Z in calculation)
The peak voltage across C_1 : 19,813V	The average voltage across C_1 : 18,919V
The current through R_s : 59,46mA	The collector current of Q_1 : 780,54mA
The base current of Q_1 : 19,46mA	The emitter current of (Q_1): 800mA
The power wasted in R_s : 530,324mW	The power wasted in Z_1 : 400mW
The power wasted in Q_1 : 7,508W ($V_{CE} \times I_C$)	The zener current if the load is disconnected: 59,46mA

QUESTION 3

$$\begin{aligned} \textcircled{1} \quad V_{B_{Q_1}} &= V_{Z_1} = V_{BE_{Q_1}} + V_{R_L} \\ 10 &= 0,7 + V_{R_L} \\ V_{R_L} &= 9,3 \text{ V} \end{aligned}$$

$$\textcircled{2} \quad \cancel{V_{R_S}} = \cancel{V_{C_1}} - \cancel{V_{Z_1}}$$

$$\begin{aligned} \textcircled{2} \quad I_T &= I_{Z_1} + I_{R_L} \\ &= 40 \text{ m} + 800 \text{ m} \\ &= 840 \text{ mA} \end{aligned}$$

$$\begin{aligned} \textcircled{3} \quad V_{r(p-p)} &= \frac{I}{C_F} \\ &= \frac{840 \text{ m}}{4700 \mu \times 100} \\ &= 1,787 \text{ V} \end{aligned}$$

$$\begin{aligned} \textcircled{4} \quad V_{AB_p} &= \sqrt{2} V_{rms} \\ &= \sqrt{2} \times 15 \\ &= 21,213 \text{ V} \end{aligned}$$

$$\begin{aligned} \textcircled{5} \quad V_{C_1_p} &= V_{AB_p} - 2V_d \\ &= 21,213 - 1,4 \\ &= 19,813 \text{ V} \end{aligned}$$

$$\begin{aligned} \textcircled{6} \quad V_{C_1_{AVE}} &= V_{C_1_p} - \frac{V_{r(p-p)}}{2} \\ &= 19,813 - \frac{1,787}{2} \\ &= 18,919 \text{ V} \end{aligned}$$

$$\begin{aligned} \textcircled{7} \quad V_{R_S} &= V_{C_1} - V_{Z_1} \\ &= 18,919 - 10 \\ &= 8,919 \text{ V} \end{aligned}$$

$$\begin{aligned} \textcircled{8} \quad I_{R_S} &= \frac{V_{R_S}}{R_S} = \frac{8,919}{150} \\ &= 59,46 \text{ mA} \end{aligned}$$

$$\begin{aligned} \textcircled{9} \quad I_{R_S} &= I_{B_{Q_1}} + I_{Z_1} \\ 59,46 \text{ m} &= I_{B_{Q_1}} + 40 \text{ mA} \\ I_{B_{Q_1}} &= 19,46 \text{ mA} \end{aligned}$$

$$\begin{aligned} \textcircled{10} \quad I_{E_{Q_1}} &= I_{R_L} \\ &= 800 \text{ mA} \end{aligned}$$

$$\begin{aligned} \textcircled{11} \quad I_{E_{Q_1}} &= I_{C_{Q_1}} + I_{B_{Q_1}} \\ 800 \text{ m} &= I_{C_{Q_1}} + 19,46 \text{ m} \\ I_{C_{Q_1}} &= 780,54 \text{ mA} \end{aligned}$$


$$\begin{aligned} \textcircled{12} \quad P_{R_S} &= V_{R_S} I_{R_S} = 8,919 \times 59,46 \text{ m} \\ &= 530,324 \text{ mW} \end{aligned}$$

$$\begin{aligned} \textcircled{13} \quad P_{Z_1} &= V_{Z_1} I_{Z_1} = 10 \times 40 \text{ m} \\ &= 400 \text{ mW} \end{aligned}$$

$$\begin{aligned} \textcircled{14} \quad V_{CE_{Q_1}} &= V_{C_1} - V_{R_L} \\ &= 18,919 - 9,3 \\ &= 9,619 \text{ V} \end{aligned}$$

$$\begin{aligned} \textcircled{15} \quad P_{Q_1} &= V_{CE_{Q_1}} I_{C_{Q_1}} \\ &= 9,619 \times 780,54 \text{ m} \\ &= 7,508 \text{ W} \end{aligned}$$

$$\textcircled{16} \quad I_{2 \text{ NO LOAD}} = I_{R_S} = 59,46 \text{ mA}$$

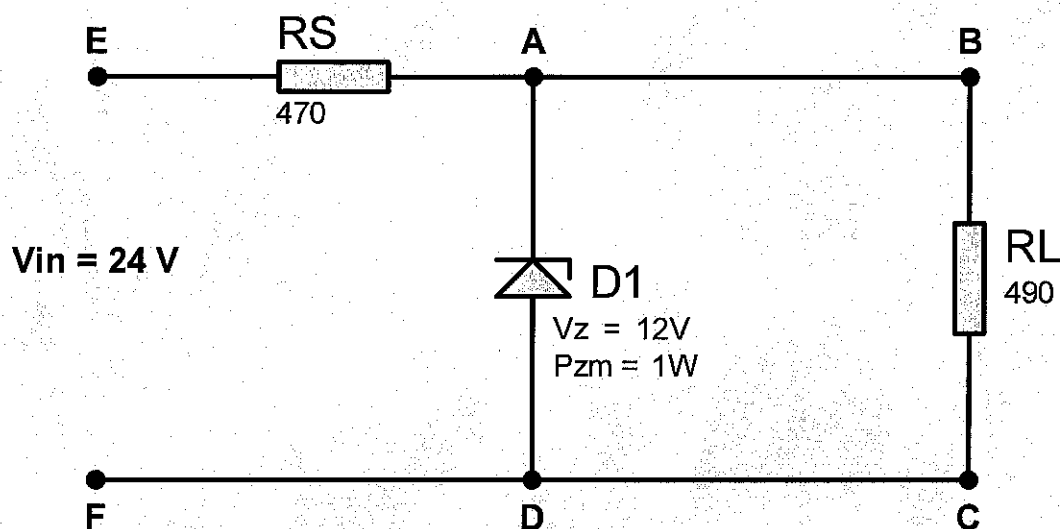QUESTION 4 (9)

Fill in the table below

	Answer
Voltage across R_S	12 V
Current through R_S	25,532 mA
Voltage across $D1$	12 V
Current through $D1$	1,042 mA
Voltage across R_L	12 V
Current through R_L	24,49 mA
Power dissipated in R_S	306,384 mW
Power dissipated in R_L	293,88 mW
Power dissipated in $D1$	12,504 mW

QUESTION 4.

4.

$$\textcircled{1} V_{in} = V_{RS} + V_Z$$

$$24 = V_{RS} + 12$$

$$V_{RS} = 12 \text{ V}$$

$$\textcircled{2} I_{RS} = \frac{V_{RS}}{R_S} = \frac{12}{470} = 25,532 \text{ mA}$$

$$\textcircled{3} V_{D1} = V_Z = 12 \text{ V}$$

$$\textcircled{4} I_{RS} = I_{D1} + I_{RL}$$

$$\textcircled{5} V_{RL} = V_{D1} = 12 \text{ V}$$

$$\textcircled{6} I_{RL} = \frac{V_{RL}}{R_L} = \frac{12}{490} = 24,49 \text{ mA}$$

$$\textcircled{7} I_{RS} = I_{D1} + I_{RL}$$

$$25,532 \text{ mA} = I_{D1} + 24,49 \text{ mA}$$

$$I_{D1} = 1,042 \text{ mA}$$

$$\textcircled{8} P_{RS} = V_{RS} I_{RS}$$

$$= 12 \times 25,532 \text{ m}$$

$$= 306,384 \text{ mW}$$

$$\textcircled{9} P_{RL} = V_{RL} I_{RL}$$

$$= 12 \times 24,49 \text{ m}$$

$$= 293,88 \text{ mW}$$

$$\textcircled{10} P_{D1} = V_{D1} I_{D1}$$

$$= 12 \times 1,042 \text{ m}$$

$$= 12,504 \text{ mW}$$