



Tshwane University of Technology

We empower people

Department of Computer Systems Engineering

EL2116D/ELC211B – Electronics II

20 NOV 2021 Formative Assessment

Total Marks: 51

Full Marks: 45

Time: 2 Hours

Examiner: Mr. T Matshiba

Mr. A. Mpiana

Moderator: Mrs Z Mahlobogwane

MEMO

Surname, initials:

Student number:

m e m o

Instructions:

- All exam rules stated by the Tshwane University of Technology applies.
- This is a **closed-book test**. You are not allowed to use any notes or text books to assist you to answer the questions.
- **Write your answer in the space provided on the question paper. Show all calculations.** Do all calculations on the counter clear page of the questionnaire if extra space is needed. Handwriting should be neat and readable. Untidy work will not be marked.
- Programmable calculators are not allowed.
- If needed, state all necessary assumptions clearly.

Question1 – Multiple Choice (10)

Each multiple choice question will count 2 mark. Choose the best suitable answer and mark with an "x" in the given table.


Multiple Choice Answer Sheet

	A	B	C	D
1				X
2			X	
3				X
4		X		
5	X			
6			X	
7				X
8		X		
9		X		
10				X

1. In a(n) _____, when the input voltage exceeds a specified reference voltage, the output changes state.


A. Integrator
B. Differentiator
C. Summing amplifier
☒ D. Comparator

2. The given circuit is known as

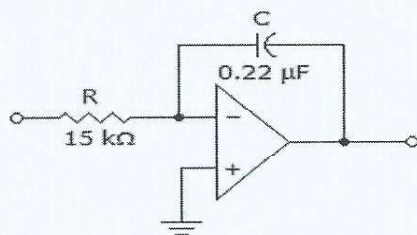


A. A noninverting amplifier.
B. A differentiator.
☒ C. An Integrator.
D. A summing amplifier.

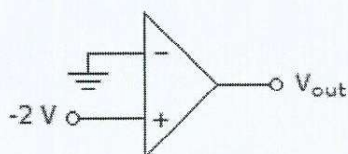3. Refer to the given circuit. What is the output voltage?




A. 2V
B. -2V
C. +Vsat
☒ D. -Vsat

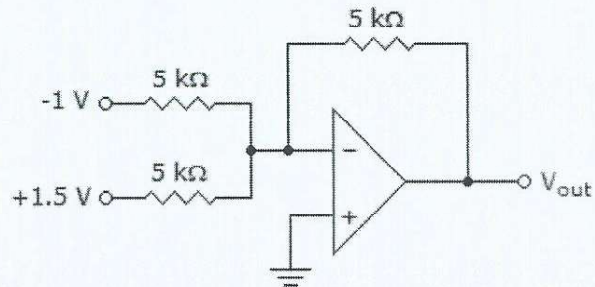4. Refer to the given circuit. What is the output voltage




- A. 0.5V
- ☒ B. -0.5V
- C. 2V
- D. -2V

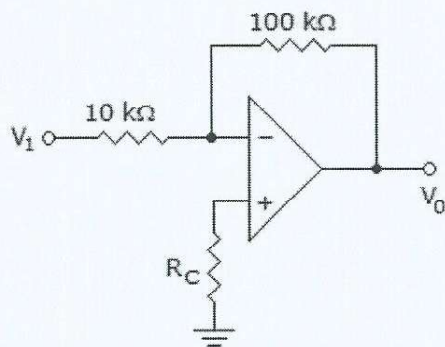5. Calculate the input voltage for this circuit if $V_0 = -11V$.



- ☒ A. 1.1V
- B. -1.1V
- C. -1V
- D. 1V

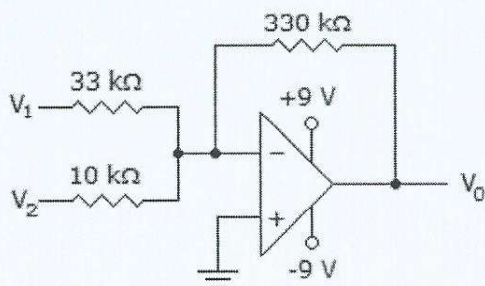6. Calculate the output voltage if $V_1 = 33mV$ and $V_2 = 2mV$.



- A. 0V
- B. -6.6V
- ☒ C. -0.4V
- D. 2V

7. How many op-amps are required to implement this equation?


$$V_0 = V_1$$

- A. 4
- B. 3
- C. 2
- ☒ D. 1

8. The gain of a noninverting amplifier can be given as

- A. $1 - R_f/R_1$
- ☒ B. $1 + R_f/R_1$
- C. $1 - R_1/R_f$
- D. $1 + R_1/R_f$

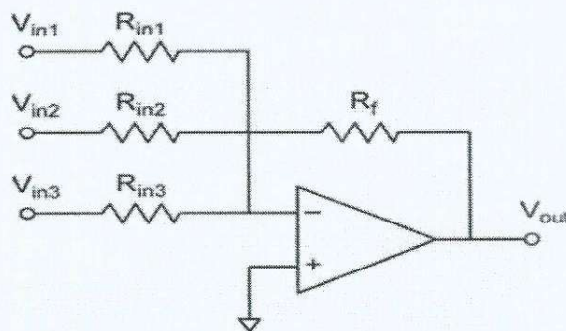9. The design of the circuit below represents



- A. an integrator amplifier
- ☒ B. a summing amplifier
- C. inverting amplifier
- D. non- inverting amplifier

10. A certain noninverting amplifier has R_i of 1 k Ω and R_f of 100 k Ω . What is the closed-loop voltage gain


- A. 100,000
- B. 1000
- C. 100
- ☒ D. 101

QUESTION 2 [7]

V1 = 1 Volt DC
V2 = 2 Volt DC
V3 = 3 Volt DC


The operational amplifiers are supplied with a split supply of +15V and -15 V

Fill in:
(Indicate polarities)

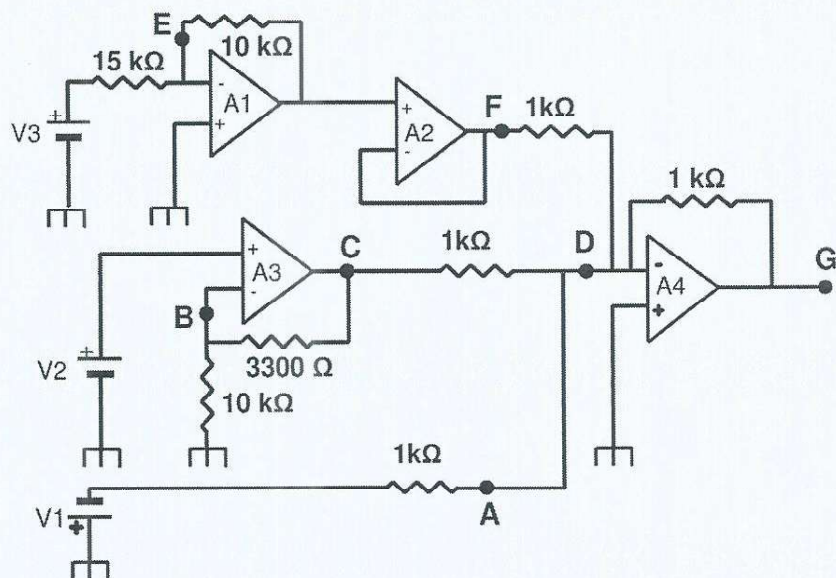

	ANSWER
The voltage at point A	0V OR Virtual Ground
The voltage at point B	+2V
The voltage at point C	+2,66V
The voltage at point D	0V
The voltage at point E	0V OR Virtual Ground
The voltage at point F	-2V
The voltage at point G	0,34V


QUESTION 3 (14)

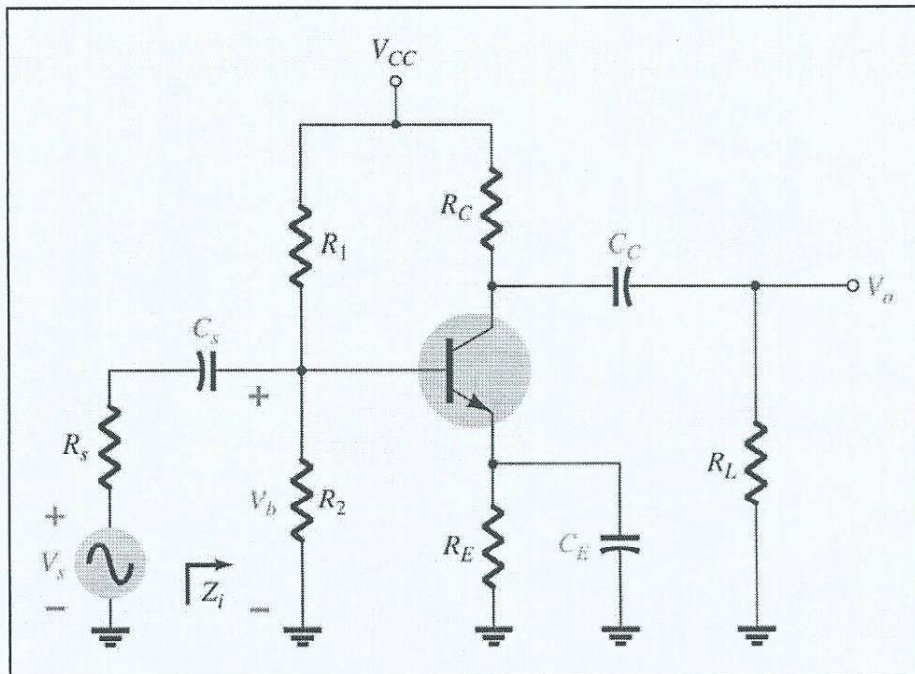

An npn transistor is used to design a common emitter amplifier such as in the figure above. The β value of the transistor is specified $\beta = 100$

$V_{CC} = 12\text{ V}$; $R_S = 100\ \Omega$; $R_L = 10\text{ k}\Omega$; $R_C = 1.5\text{ k}\Omega$; $R_E = 2\text{ k}\Omega$; $R_1 = 33\text{ k}\Omega$; $R_2 = 22\text{ k}\Omega$

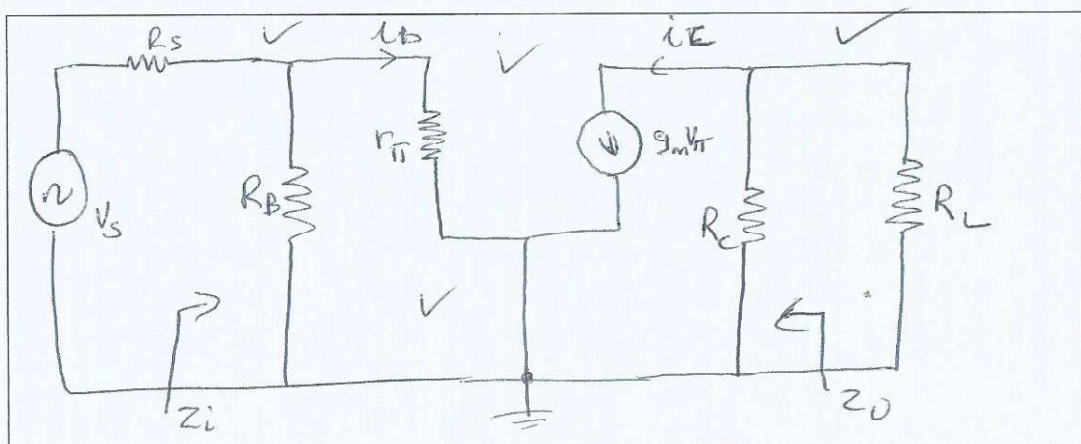- a) DRAW the ac small-signal equivalent circuit (π -parameters) or (h-parameters). (4)



- b) Calculate the value of Z_i (6)
 c) Calculate the Voltage Gain $A_{V(NL)}$ with R_L disconnected (open circuit) (2)
 d) Calculate the Voltage Gain A_V with R_L connected. (2)

Show all calculations

b) $Z_V = ?$

$$\begin{aligned} \textcircled{1} V_{R_2} &= 12 \times \frac{22\text{K}}{33\text{K} + 22\text{K}} \\ &= 4,8\text{V} \quad \checkmark \end{aligned}$$

$$\begin{aligned} \textcircled{2} V_{RE} &= V_{R_2} \approx V_{BE} \\ &= 4,8 - 0,7 \\ &= 4,1\text{V} \end{aligned}$$

$$\begin{aligned} \textcircled{3} R_B &= R_1 \parallel R_2 \\ &= 33\text{K} \parallel 22\text{K} \\ &= 13,2\text{K} \quad \checkmark \end{aligned}$$

$$\begin{aligned} \textcircled{4} I_E &= \frac{V_{BB} - V_{BE}}{R_E + \frac{R_B}{\beta + 1}} \\ &= \frac{4,8 - 0,7}{2\text{K} + \frac{13,2\text{K}}{100 + 1}} \\ &= \frac{4,1}{2,13\text{K}} \\ &= 1,925\text{mA} \quad \checkmark \end{aligned}$$

$$\textcircled{5} I_C \approx I_E = 1,925$$

$$\begin{aligned} \textcircled{6} r_{\pi} &= \frac{V_T \beta}{I_C} \\ &= \frac{25\text{m} \times 100}{1,925\text{m}} \quad \checkmark \\ &= 1298,7\Omega \end{aligned}$$

$$\begin{aligned} \textcircled{7} Z_{in} &= R_B \parallel r_{\pi} \quad \checkmark \\ &= 13200 \parallel 1298,7 \\ &= 1182,37\Omega \\ &= 1,182\text{K}\Omega \quad \checkmark \end{aligned}$$

$$\begin{aligned} \textcircled{8} A_{V_{ML}} &= -g_m R_C \quad \checkmark \\ \text{but } g_m &= \frac{I_C}{V_T} = \frac{1,925\text{m}}{25\text{m}} \\ &= 0,077 \end{aligned}$$


$$\begin{aligned} \therefore A_{V_{ML}} &= -0,077 \times 1,5\text{K} \\ &= -115,5 \quad \checkmark \end{aligned}$$

$$\begin{aligned} \textcircled{9} A_{V_L} &= -g_m R_L' \quad \checkmark \\ &= -g_m (R_C \parallel R_L) \\ &= -0,077 \times (1304) \\ &= -100,4 \quad \checkmark \end{aligned}$$

OR

$$\begin{aligned} A_{V_L} &= A_{V_{ML}} \frac{R_L}{R_C + R_L} \\ &= -115,5 \frac{10\text{K}}{1,5\text{K} + 10\text{K}} \\ &= 100,4 \end{aligned}$$

QUESTION 4 [12]

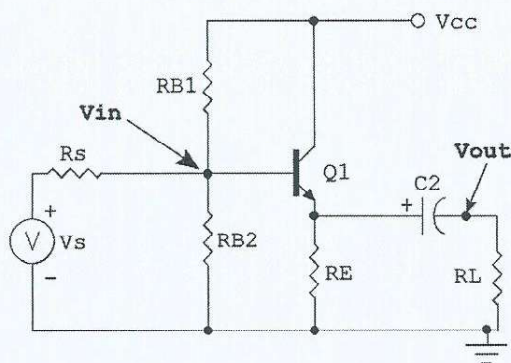

Given: $r'e = 25\text{mV} \div I_E$; $r_{\pi} = \beta \times r'e$;

$I_E = 1,914 \text{ mA}$

$R_{B1} = 27 \text{ k}\Omega$; $R_{B2} = 15 \text{ k}\Omega$; $R_s = 2 \text{ k}\Omega$;


$R_L = 500 \Omega$; $R_E = 1.5 \text{ k}\Omega$

$V_{CC} = +10 \text{ V}$; $\beta = 280$

Assuming all capacitors and the DC power supply (V_{CC}) represent a zero ohm reactance at the ac signal,

a) **DRAW** the complete small-signal equivalent circuit.

(4)

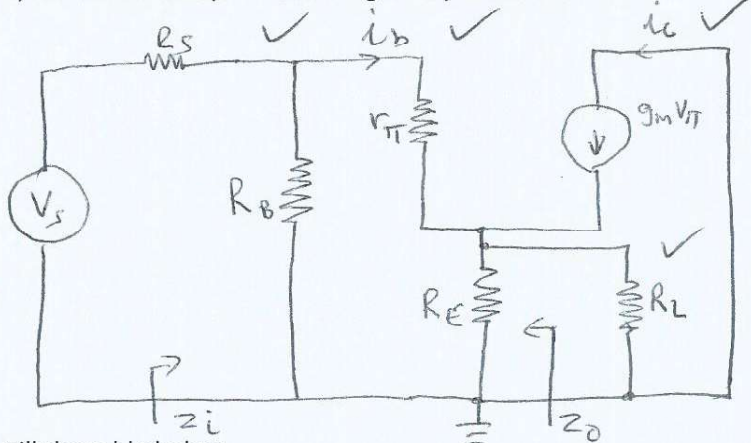


Fill the table below

$r_{\pi} =$ 3657Ω $3,657 \text{ k}\Omega$		In what amplifier configuration is the circuit connected? common collector	
Z_i (include loading of R_L) = 8859Ω $8,859 \text{ k}\Omega$		Z_o (exclude R_L) = $45,88 \Omega$	
Voltage gain between V_o and V_i :	0,966	Voltage gain between V_o and V_s :	0,788
Voltage gain in dB between V_o and V_s : Given: $\text{dB} = 20 \log V_o / V_s$			-2,069 dB
If $V_s = 100 \text{ mV RMS}$, what is the magnitude of V_o (in RMS)?			78,8 mV

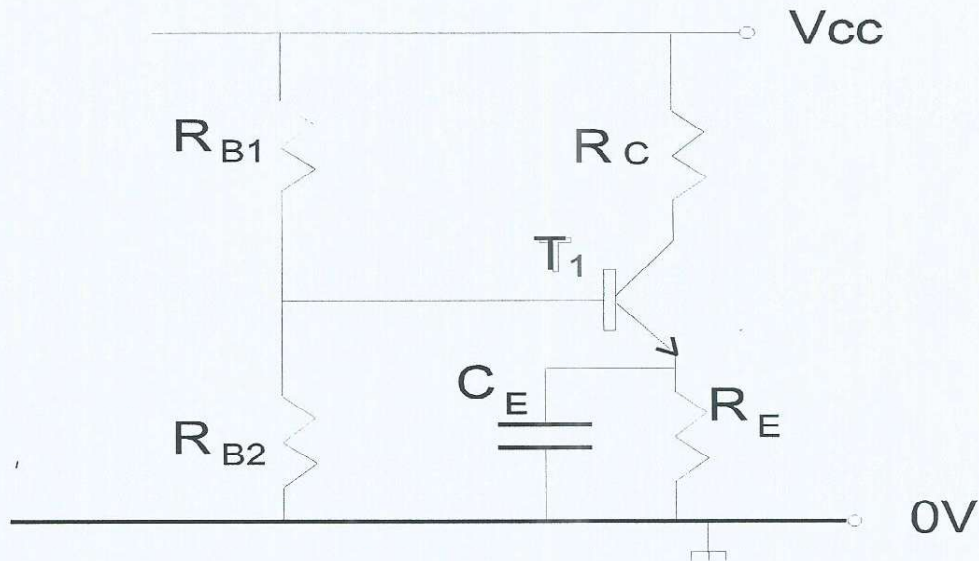QUESTION 5 [8]

Perform only the DC (steady state) analysis in the following circuit:

$V_{BE} = 0,7 \text{ V}$, $R_{B1} = 24\text{k}\Omega$, $R_{B2} = 5\text{k}\Omega$, $R_E = 1\text{k}\Omega$, $R_C = 3\text{k}\Omega$, $V_{CC} = 15\text{V}$, $\beta = 250$



The average voltage across R_{B2} (V_{RB2})	2,838 V
The average voltage across R_E (V_{RE})	2,138 V
The average current through R_E (I_E)	1,425 mA
The average voltage across R_{B1} (V_{RB1})	12,162 V
The average voltage across T_1 (V_{CE})	8,179 V
The average voltage at the collector V_C	10,317 V
The average voltage across R_C (V_{RC})	4,683 V
The average current through collector (I_C)	1,419 mA